

SASP Homework Assignment No. 2 (HWA2)

Mattia Montanari, Flavio Ingenito

- 1st series adaptor (to compensate input voltage source and the 1st capacitor):

$$Z_{10} = Z_{11} + Z_{12}$$

- 2nd series adaptor (to compensate the resistance):

$$Z_7 = Z_8 + Z_9$$

- 1st parallel adaptor (to adapt the diodes with the rest of the circuit):

$$Z_3 = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

- 2nd parallel adaptor (to compensate the output resistance and the 2nd capacitor):

$$Z_4 = \frac{Z_5 Z_6}{Z_5 + Z_6}$$

Finally it comes the setting of the free-parameters to connect the four adaptors together

- Connecting 1st series adaptor with the 2nd one

$$Z_8 = Z_{10}$$

- Connecting 2nd series adaptor with the 1st parallel one

$$Z_2 = Z_7$$

- Connecting 1st parallel adaptor with the 2nd one

$$Z_1 = Z_4$$

0.2 Plots of the results

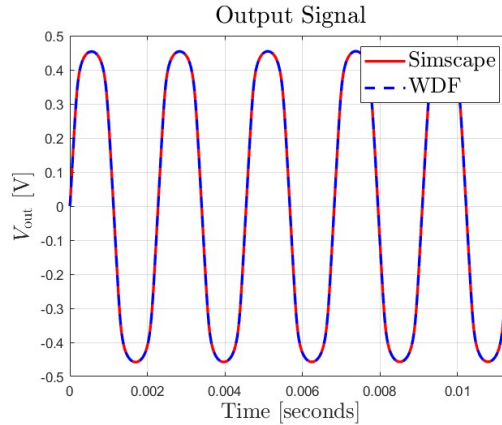


Figure 2. Plot of the output signal compared with the ground-truth provided as reference. As it is possible to see, the 2 signal are almost perfectly superimposed.

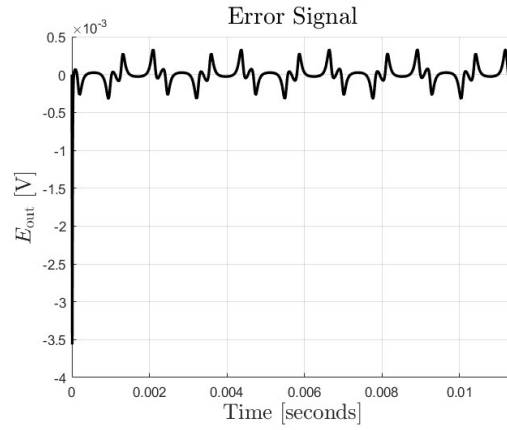


Figure 3. Plot of the error signal, namely the difference between our output signal and the ground-truth provided as reference. In this plot is shown the evolution of the error over time but considering a mean value, the overall Mean Square Error is equal to $2.0941\text{e-}07$.

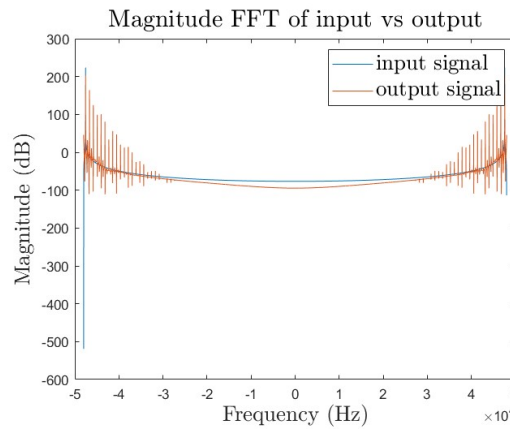


Figure 4. Plot of the spectrum of the input signal compared with the one of the output. From this plot it's clearly noticeable the effect of the distortion since there are new harmonic components on the output signal.